


1 bit Memory Element

Uses D flip flop to store 1 bit data in memory.

Construction:

RS Latch:

1. Block Diagram:

 


2. Verilog Code:

```
module RS1 (output reg q, output reg qn, input r, input s);  
  
    // rs latch modeling  
    always @(q, qn, r, s) begin  
        q <= ~ (qn | r);  
        qn <= ~ (q | s);  
    end  
  
endmodule
```

D Latch using RS Latch:

1. Block Diagram:

 


2. Verilog Code:

```
module D1 (output q, output qn, input d, input clk);  
  
    reg r, s;  
  
    // using rs latch module  
    RS1 RS1instD1 (q, qn, r, s);  
  
    // d latch modelling  
    always @ (r, s, d, clk) begin  
        r <= (~ d) & clk;  
        s <= d & clk;  
    end  
  
endmodule
```

D flip-flop using master slave D Latch:

1. Block Diagram:

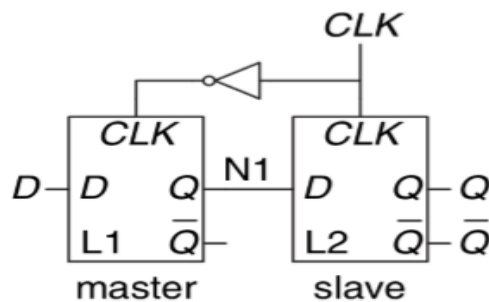

2. Verilog Code:

```
module Dff (output q, output qn, input d, input clk, input res);  
  
    reg nclk;  
    wire qi, qni;  
  
    // active low reset signal  
    wire new_d;  
    assign new_d = d & res;  
  
    // D latch 1  
    D1 inst1 (qi, qni, new_d, nclk);  
    // D latch 2  
    D1 inst2 (q, qn, qi, clk);  
  
    // complement of clock  
    always @ (clk) begin  
        nclk <= ~clk;  
    end  
  
endmodule
```

Explanation:

Using the above block diagrams each module is coded and used as blocks in other modules.

It helps to store 1 bit data in memory along with a active low reset signal. The master slave configuration allows the sequential circuit to be positive edge triggered.