

# Adder and Subtractor (n-bit) using a single full adder

## Adder

n bit adder can be made using a for loop

```
n1=3;
n2=9;
imm=0;
op1=1'b0;
op2=1'b0;
op3=1'b0;
$display("Calculating %d+%d",n1,n2);
$display("Bits from LSB to MSB in order are as follows");
// 3 can be replaced by x
for (i=0;i<=3;i=i+1) begin


    #10    op1=n1[i];
           op2=n2[i];
           op3=imm;
           assign imm=carry;
           // Displaying the sum bit
           #10    $display("%b",sum);
end
// displaying the extra bit (it will be 1 if necessary)
$display("%b",carry);
$finish;
```

end

The full adder starts adding bits (starting from the least significant bit) and the carry is stored in a intermediate variable 'imm'. Hence, using a single adder multiple bits can be added.

To change the number of bits the size of array and the limits in for loop must be changed in the test bench.

## Subtractor

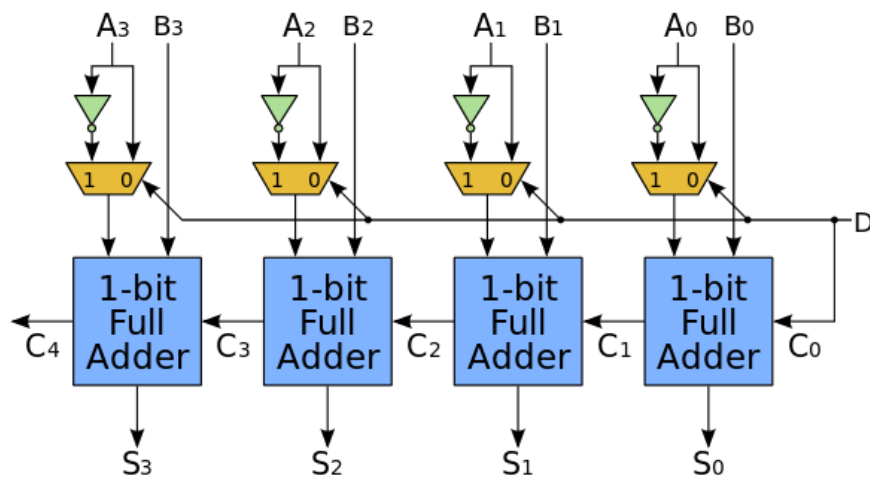

Adder can be modified into a subtractor by negating the input bits and changing the initial carry to 1.

Rest of addition can be done using a for loop.

```
$dumpvars(0, t_Subtractor);
n1=7;
n2=2;
imm=1;
op1=1'b0;
op2=1'b0;
op3=1'b0;
$display("Calculating %d-%d\nResult in 2's complement",n1,n2);
$display("Bits from LSB to MSB in order are as follows");
// 3 can be replaced by x
for (i=0;i<=3;i=i+1) begin
    #10    op1=n1[i];
           op2=~(n2[i]);
           op3=imm;
           assign imm=carry;
           // Displaying the sum bit
           #10    $display("%b",sum);
end
// End of the program
```

Just like in the case of adder.